

**AUTOMATIC SYNTHESIS OF
ELECTRICAL CIRCUITS USING
DEVELOPMENTAL GENETIC
PROGRAMMING**

PART 1 — METHODS

OUTLINE

- **The design process**
- **Circuit Synthesis using developmental genetic programming**
 - Initial circuit (embryo plus test fixture)
 - Circuit-constructing program trees
 - Component-creating functions
 - Topology-modifying functions
 - Development-controlling functions

EXAMPLES

- **Filters (lowpass, highpass, bandpass bandstop)**
- **Filters (Campbell, Zobel, Johnson, Butterworth, Chebychev, Cauer [elliptic])**
- **Crossover filters (woofer-tweeter, woofer-midrange-tweeter)**
- **Source Identification Problem (three-way and four-way — with changing environment)**
- **Amplifiers (10 dB, 40 dB, 60 dB, 96 dB)**
- **Computational circuits (squaring, cubing, square root, cube root, logarithmic, Gaussian)**
- **Circuit for time-optimal fly-to controller**
- **Temperature-sensing circuit**
- **Voltage reference circuit**
- **Philbrick circuit**
- **NAND gate**
- **Digital-to-analog converter (DAC)**
- **6 post-2000 patented inventions**

DESIGN

- **Find a structure, composed of components of various types, that satisfies user-specified goals**
- **Design is a major activity of practicing engineers**
- **The design process typically entails tradeoffs between competing considerations**
- **The end product of the design process is usually a satisfactory and compliant design as opposed to a perfect design**
- **Design is usually viewed as requiring human intelligence**

DESIGN USING GENETIC PROGRAMMING

- **Can be done with a minimum of domain-specific knowledge and no mathematical analysis, abstractions, or formal models**
- **Starts with a set of ingredients and information concerning the number of inputs and outputs**
- **Is driven by the user's design goals (implemented as a single scalar "fitness" value).**
- **It's (almost) WYWIWYG – “What You Want Is What You Get” (pronounced “wow-eee-wig”)**
- **However, as they, be careful what you ask for because the process is, more precisely, WYGIWYAF – “What You Get Is What You Ask For”**

THE SEARCH SPACE FOR EVEN A SIMPLE ELECTRICAL CIRCUIT IS VERY LARGE

ASSUMPTIONS FOR ILLUSTRATIVE EXAMPLE

- Assume only a one-input, one-output circuit
- Assume we know exact size of ultimate circuit in advance and that it is only 20 components (Note: the number of components is, in general, unknowable in advance and 20 is small)
- Assume only two-leaded components
- Assume only 3 types of such components: Resistor (R), Capacitor (C), Inductor (I)
- Assume only 20 component values per decade (i.e., dividing each decade into 5% slices) and 10 decades of component values (i.e., a total of only 200 possible values)

LARGE SEARCH SPACE FOR EVEN A SIMPLE ELECTRICAL CIRCUIT - CONTINUED

- The calculation below is overly simplified, but suggestive of large size of the search space
- Then, given the above assumptions, there are 861 ways of choosing two leads from 42 leads ($20 \times 2 + 2 = 42$) and thus a total of 2^{861} ($\sim 10^{260}$) ways of making undirected connections between two leads
- There are 3^{20} ($\sim 10^9$) possible ways of picking the type of component
- There are 200^{20} ($\sim 10^{52}$) possible ways of the value of each of the 20 components
- Thus, there are approximately up to 10^{321} possible circuits with exactly 20 components (and with the above assumptions)
- And, of course, one would rarely know, in advance, that the requisite circuit had precisely 20 components


DIFFICULTY OF AUTOMATED ANALOG CIRCUIT DESIGN

- ***Analysis* of a circuit is itself difficult, and there is no previous general way to automate the *synthesis* of an analog electrical circuit from a high-level statement of the circuit's behavior and characteristics**
- **A hard problem**
 - Exponential in the number of components
 - More than 10^{300} circuits with a mere 20 components

DIFFICULTY OF AUTOMATED ANALOG CIRCUIT DESIGN — CONTINUED


- **An important problem**
 - Too few analog designers
 - There is a comparatively small "egg shell" of analog circuitry around almost all digital circuits
 - The time required for the total design is often controlled by the time required to design the analog portion
 - Analog circuits must be redesigned with each new generation of solid-state process technology
 - Solid-state process technology is optimized for digital circuits – thus making analog design even more difficult

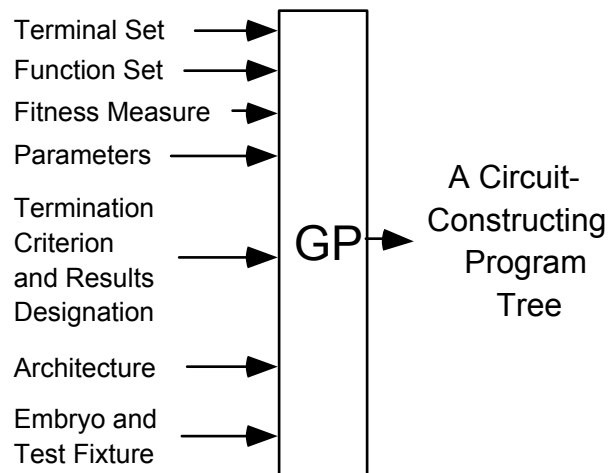DEVELOPMENTAL GENETIC PROGRAMMING FOR AUTOMATED SYNTHESIS OF ANALOG CIRCUITS




ONE-INPUT, ONE-OUTPUT INITIAL CIRCUIT

 - Initial circuit consists of embryo and test fixture
- Embryo has modifiable wires (e.g., **Z0** AND **Z1**)
- Test fixture has input and output ports and usually has source resistor and load resistor. There are no modifiable wires (or modifiable components) in the test fixture.




THE INITIAL CIRCUIT

 - **Circuit-constructing program tree contains**
 - Component-creating functions
 - Topology-modifying functions
 - Development-controlling functions
- **Circuit-constructing program tree has one result-producing branch for each modifiable wire in embryo of the initial circuit**
- **There is a writing head linking each modifiable wire (or modifiable component) with one point of the program tree**




TWO PARTS OF AN INITIAL CIRCUIT

 EMBRYO WITH TWO MODIFIABLE WIRES, Z0 AND Z1 AND THREE PORTS (EMBRYO_INPUT, EMBRYO_OUTPUT, AND EMBRYO_GROUND)



TWO PARTS OF AN INITIAL CIRCUIT

 ONE-INPUT, ONE-OUTPUT TEST FIXTURE WITH THREE PORTS TO THE EMBRYO



TWO PARTS OF AN INITIAL CIRCUIT

THE EMBRYO

- **An embryo contains at least one modifiable wire. A modifiable wire is a wire that is capable of being converted into electrical components, other modifiable wires, and nonmodifiable wires during the developmental process.**
- **The embryo is very simple - often as little as one (or a few) modifiable wires**
- **An embryo has one or more ports that enable it to be embedded into a test fixture.**
- **When the embryo is embedded in the test fixture, the result is typically a useless and degenerate circuit**

TWO PARTS OF AN INITIAL CIRCUIT

THE EMBRYO - CONTINUED

- **Occasionally, an embryo may also contain non-modifiable wires, non-modifiable electrical components, or modifiable electrical components.**
- **The developmental process operates on the embryo (not the test fixture)**
- **The distinctive feature of the embryo is that it contains at least one modifiable wire.**

TWO PARTS OF AN INITIAL CIRCUIT

THE TEST FIXTURE

- **The test fixture is a fixed (hard-wired) substructure composed of nonmodifiable wires and nonmodifiable electrical components.**
- **Its purpose is to provide a means for testing another electrical substructure, namely the embryo.**
- **A test fixture has one or more ports that enable an embryo to be embedded into it.**
- **The test fixture provides access to the circuit's external input(s) and outputs and permits probing of the circuit's output.**

TWO PARTS OF AN INITIAL CIRCUIT

THE TEST FIXTURE - CONTINUED


- **A test fixture typically incorporates certain fixed elements that are required to test the type of circuit being designed. For example, the test fixture often contains a source resistor reflecting the reality that all sources have resistance and a load resistor representing the load that must be driven by the output.**
- **The distinctive feature of the test fixture is that it contains no modifiable wires and no modifiable components.**

DEVELOPMENTAL PROCESS

- **In the initial circuit, the test fixture encases only the embryo.**
- **The developmental process operates on the embryo (not the test fixture)**
- **The developmental process applies functions in the circuit-constructing program tree to certain designated elements of the embryo (and its successors).**
- **The functions in the program tree side-effect the embryo (and its successors during the developmental process).**
- **The developmental process ends when the program tree is fully executed.**
- **After the embryo is fully developed, the test fixture encases the nontrivial substructure that is developed from the embryo.**

WRITING HEADS

 ONE-INPUT, ONE-OUTPUT INITIAL CIRCUIT WITH TWO WRITING HEADS ASSOCIATED WITH THE TWO MODIFIABLE WIRES (Z0 AND Z1) OF THE EMBRYO



COMPONENT-CREATING FUNCTIONS

TWO-LEADED

- **Resistor R function**
- **Capacitor C function**
- **Inductor L function**
- **Diode D function**
- **TWO_LEAD_OPAMP function**
- **Digital NOT function (inverter)**

THREE-LEADED

- **Transistor QT function**
- **THREE_LEAD_OPAMP function**
- **Digital AND, OR, NAND, NOR functions**


FOUR-LEADED

- **Transformer TRANSFORMER function**


FIVE-LEADED

- **FIVE_LEAD_OPAMP function**

 
A PORTION OF A CIRCUIT CONTAINING A MODIFIABLE WIRE Z0




RESULT AFTER R FUNCTION

 

RESULT AFTER **c** FUNCTION

 

RESULT AFTER **L** FUNCTION

 

NETLIST BEFORE EXECUTION OF R FUNCTION


```
C2 1 10  
C3 1 11  
Z0 2 1  
C4 2 12  
C5 2 13
```

Note: By convention, the first-listed node is the node connected to the positive lead of a two-leaded component


NETLIST AFTER EXECUTION OF R FUNCTION CREATING A 5-Ω RESISTOR

```
C2 1 10  
C3 1 11  
R1 2 1 5ohms  
C4 2 12  
C5 2 13
```



RESULT AFTER Q_{T0} FUNCTION

 


RESULT AFTER AND₀ DIGITAL GATE

  


RESULT AFTER TRANSFORMER0 FUNCTION




RESULT AFTER TWO_LEAD_OPAMP1

 


RESULT AFTER THREE_LEAD_OPAMP1 FUNCTION

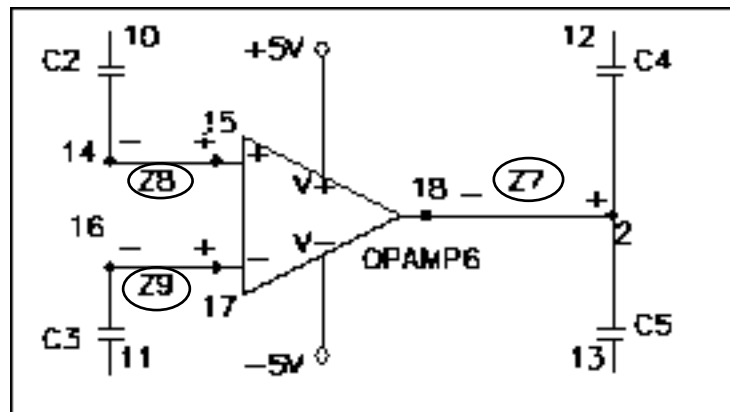


RESULT AFTER TRANSFORMER FUNCTION

 

 A PORTION OF A CIRCUIT CONTAINING A RESISTOR R1




RESULT AFTER FIVE_LEAD_OPAMP3

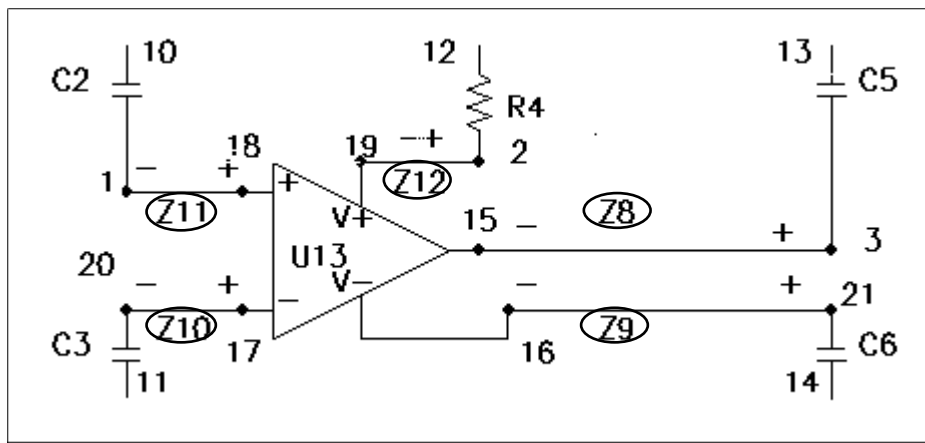


TOPOLOGY-MODIFYING FUNCTIONS

- **SERIES division function**
- **PARALLEL0 and PARALLEL1 parallel division functions**
- **STAR division function**
- **TRIANGLE division function**
- **VIA function**
- **FLIP function**

A CIRCUIT CONTAINING A RESISTOR R1

 

AFTER THE SERIES FUNCTION

 


NETLIST WITH R1

```
C2 1 10  
C3 1 11  
R1 2 1 5ohms  
C4 2 12  
C5 2 13
```


NETLIST AFTER SERIES FUNCTION

```
C2 1 10  
C3 1 11  
R1 2 4 5ohms  
Z6 4 3  
R7 3 1 5ohms  
C4 2 12  
C5 2 13
```



AFTER PARALLELO PARALLEL DIVISION

 


AFTER PARALLEL1 PARALLEL DIVISION

  


AFTER STAR1 FUNCTION




AFTER TRIANGLE1 FUNCTION

 


A CIRCUIT CONTAINING A RESISTOR R1

 


AFTER VIA0 FUNCTION

 

A CIRCUIT CONTAINING A DIODE D1

 


AFTER THE FLIP FUNCTION

 

DEVELOPMENT-CONTROLLING FUNCTIONS

- **END function**
- **NOP (No Operation) function**

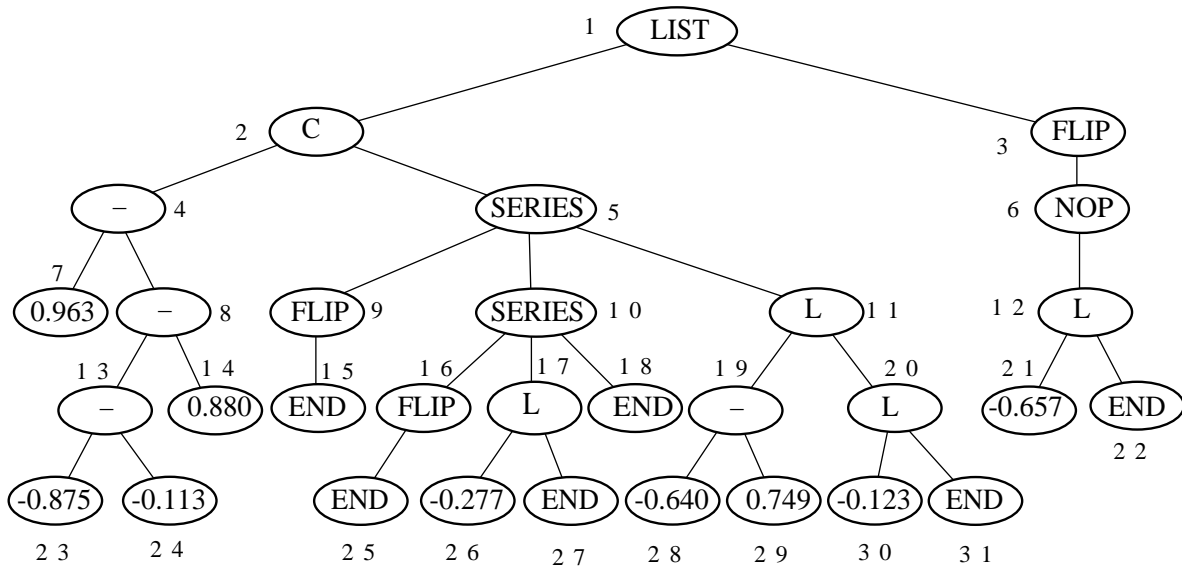A CIRCUIT FROM A CIRCUIT-CONSTRUCTING PROGRAM TREE



HIGHLIGHTED ARITHMETIC-PERFORMING SUBTREES


```
(LIST (C (- 0.963 (- (- -0.875 -0.113) 0.880)) (series (flip end) (series (flip end) (L -0.277 end) end) (L (- -0.640 0.749) (L -0.123 end)))) (flip (nop (L -0.657 end))))
```

FUNCTIONS AND TERMINALS FOR ARITHMETIC-PERFORMING SUBTREES

| Name | Short Description | Arity |
|--|---|---------|
| \mathfrak{R} | Random constants | 0 |
| + | Addition | 2 |
| - | Subtraction | 2 |
| ADF ₀ , ADF ₁ ,... | Automatically defined function 0, etc. | Various |
| ARG ₀ , ARG ₁ ,... | Dummy argument 0 (formal parameter 0), etc. | 0 |

LOGARITHMIC INTERPRETATION OF ARITHMETIC-PERFORMING SUBTREES

 - The arithmetic-performing subtree produces floating-point number X .
- X is used to produce an intermediate value U in the range of -5 to $+5$.




- If the return value X is between -5.0 and $+5.0$, an intermediate value U is set to the value X returned by the subtree.
- If the return value X is less than -100 or greater than $+100$, U is set to a saturating value of zero.
- If the return value X is between -100 and -5.0 , U is found from the straight line connecting the points $(-100, 0)$ and $(-5, -5)$.
- If the return value X is between $+5.0$ and $+100$, U is found from the straight line connecting $(5, 5)$ and $(100, 0)$.

POTENTIAL FUNCTIONS AND TERMINALS FOR AUTOMATICALLY DEFINED FUNCTIONS


| Name | Short Description | Range of Arity |
|----------|--|------------------|
| ADF- i | Automatically defined function i | 0 to MAX_{adf} |
| ARG- i | Dummy variable i (formal parameter) of automatically defined function(s) | 0 to MAX_{arg} |

DEVELOPMENT OF A CIRCUIT FROM A CIRCUIT-CONSTRUCTING PROGRAM TREE AND THE INITIAL CIRCUIT

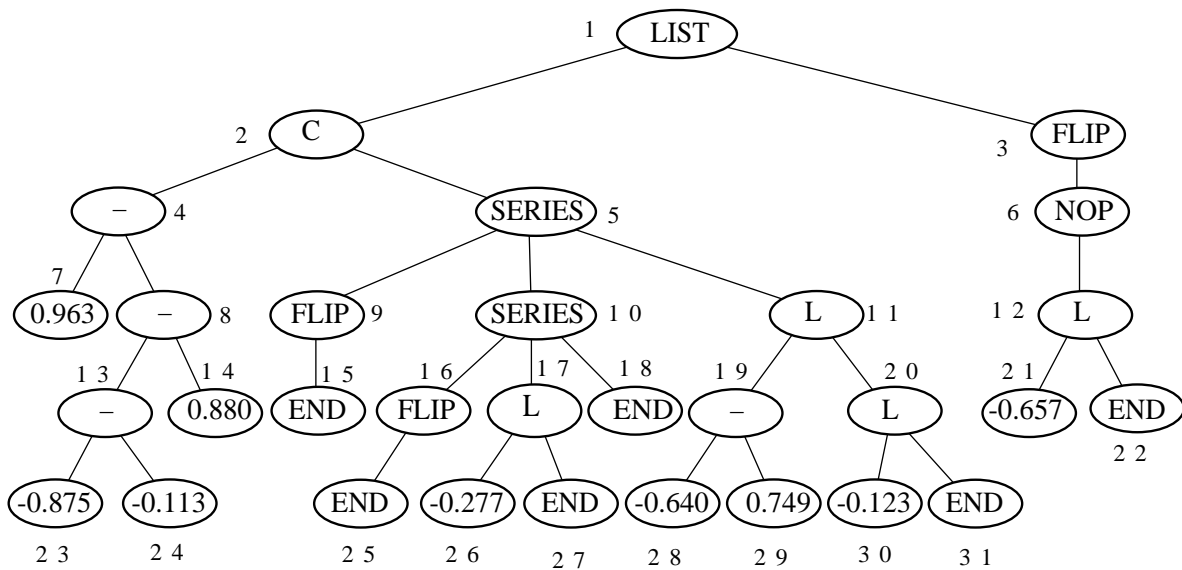
```
(LIST (C (- 0.963 (- (- -0.875 -0.113)
0.880)) (series (flip end) (series (flip
end) (L -0.277 end) end) (L (- -0.640
0.749) (L -0.123 end)))) (flip (nop (L -
0.657 end))))))
```



INITIAL CIRCUIT WITH TWO WRITING HEADS

 


RESULT OF THE c (2) FUNCTION

 

```
(LIST (C (- 0.963 (- (- -0.875 -0.113)
0.880)) (series (flip end) (series (flip
end) (L -0.277 end) end) (L (- -0.640
0.749) (L -0.123 end)))) (flip (nop (L -
0.657 end))))))
```


NOTE: Interpretation of arithmetic value

 RESULT OF THE FLIP (3) – IN 2nd RESULT-PRODUCING BRANCH




```
(LIST (C (- 0.963 (- (- -0.875 -0.113)
0.880)) (series (flip end) (series (flip
end) (L -0.277 end) end) (L (- -0.640
0.749) (L -0.123 end)))) (flip (nop (L -
0.657 end))))))
```

RESULT OF SERIES (5) FUNCTION

 


```
(LIST (C (- 0.963 (- (- -0.875 -0.113)
0.880)) (series (flip end) (series (flip
end) (L -0.277 end) end) (L (- -0.640
0.749) (L -0.123 end)))) (flip (nop (L -
0.657 end))))))
```

RESULT OF THE FLIP (9) FUNCTION

 


```
(LIST (C (- 0.963 (- (- -0.875 -0.113)
0.880)) (series (flip end) (series (flip
end) (L -0.277 end) end) (L (- -0.640
0.749) (L -0.123 end)))) (flip (nop (L -
0.657 end))))))
```

RESULT OF SERIES (10) FUNCTION

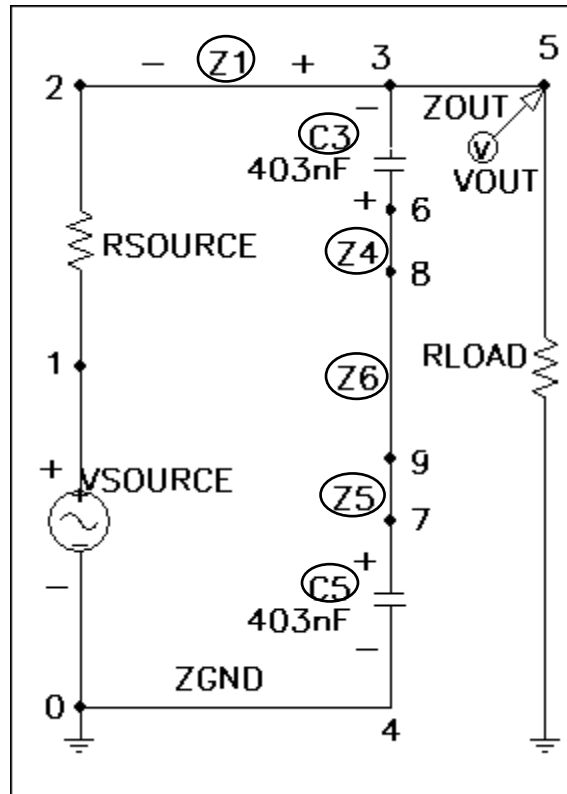


```
(LIST (C (- 0.963 (- (- -0.875 -0.113)
0.880)) (series (flip end) (series (flip
end) (L -0.277 end) end) (L (- -0.640
0.749) (L -0.123 end)))) (flip (nop (L -
0.657 end))))))
```


RESULT OF \mathcal{L} (11) FUNCTION

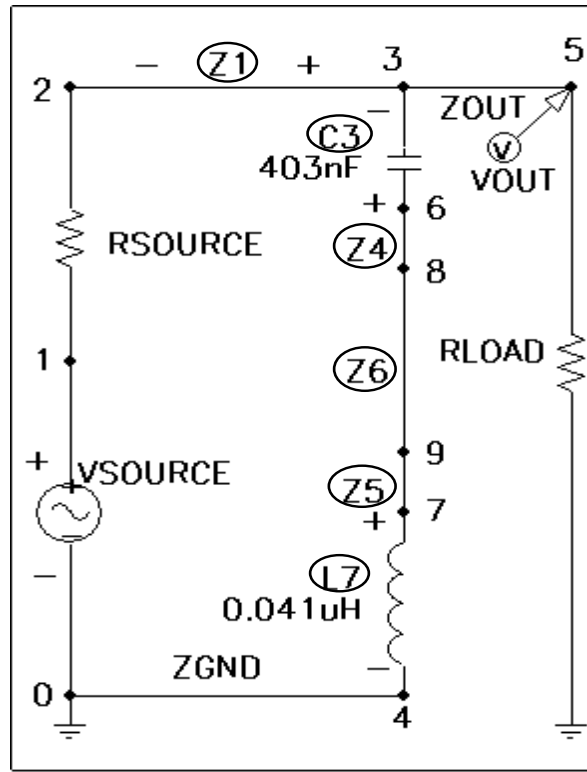


```
(LIST (C (- 0.963 (- (- -0.875 -0.113)
0.880)) (series (flip end) (series (flip
end) (L -0.277 end) end) (L (- -0.640
0.749) (L -0.123 end)))) (flip (nop (L -
0.657 end))))))
```

RESULT OF \mathcal{L} (12) FUNCTION

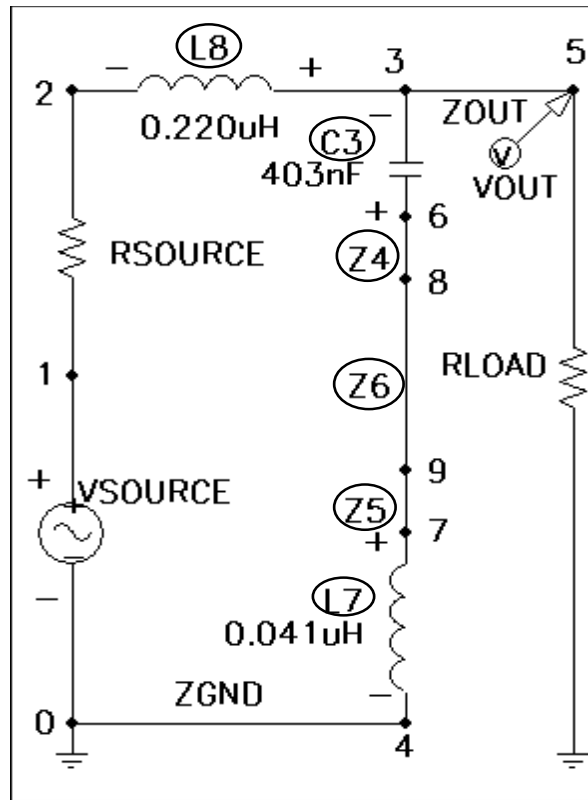


```
(LIST (C (- 0.963 (- (- -0.875 -0.113)
0.880)) (series (flip end) (series (flip
end) (L -0.277 end) end) (L (- -0.640
0.749) (L -0.123 end)))) (flip (nop (L -
0.657 end))))))
```

RESULT OF L (17) FUNCTION

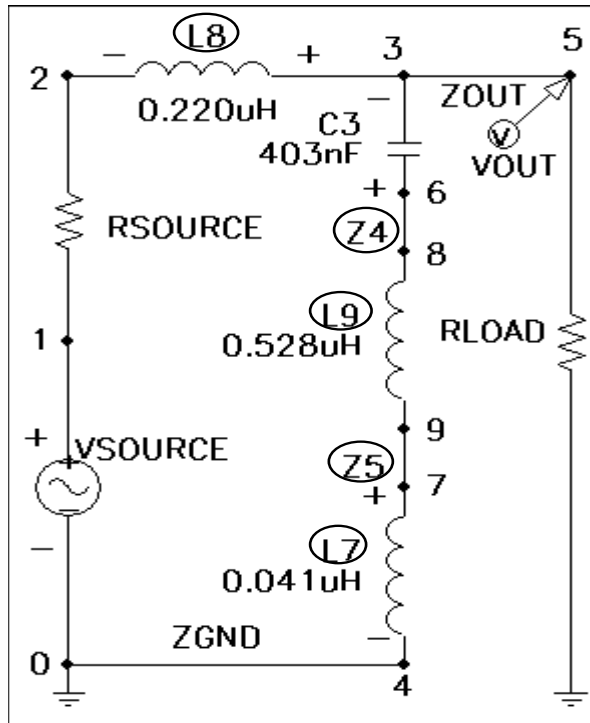


```
(LIST (C (- 0.963 (- (- -0.875 -0.113)
0.880)) (series (flip end) (series (flip
end) (L -0.277 end) end) (L (- -0.640
0.749) (L -0.123 end)))) (flip (nop (L -
0.657 end))))))
```

RESULT OF L (20) (OVERWRITING)

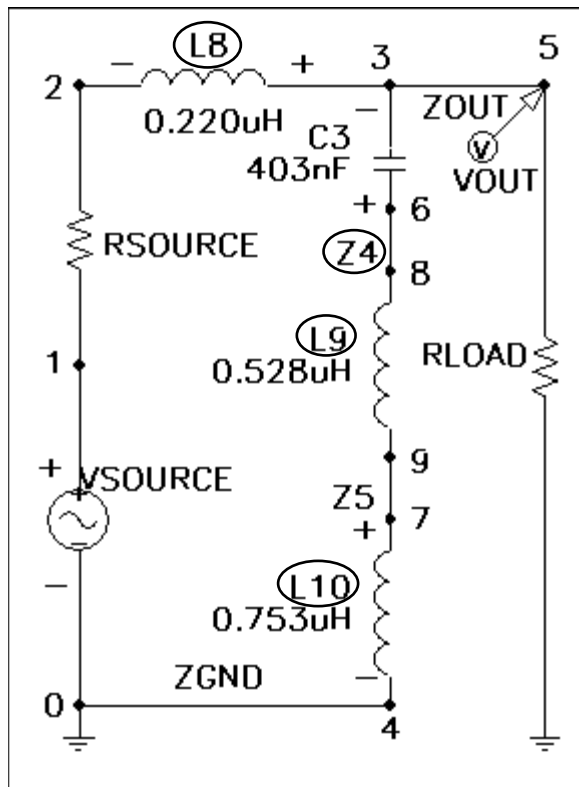


```
(LIST (C (- 0.963 (- (- -0.875 -0.113)
0.880)) (series (flip end) (series (flip
end) (L -0.277 end) end) (L (- -0.640
0.749) (L -0.123 end)))) (flip (nop (L -
0.657 end))))))
```

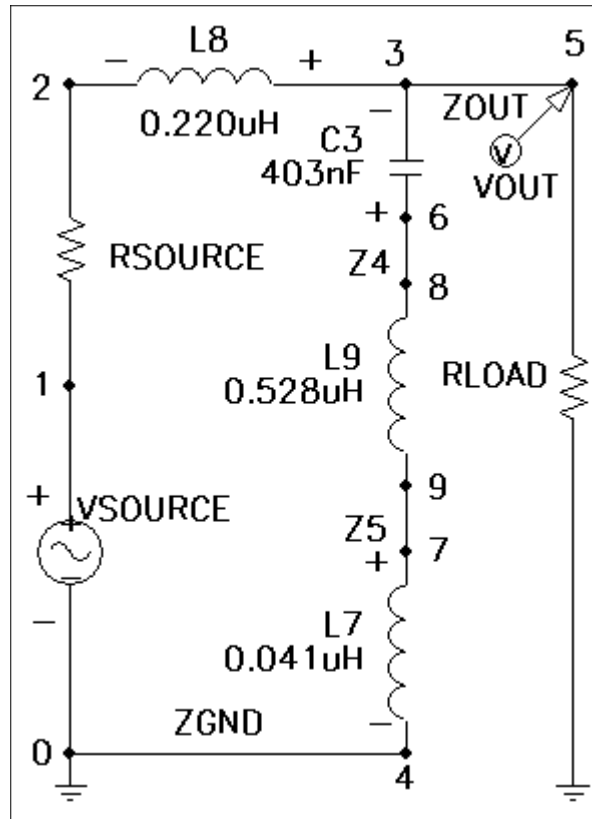THE FULLY DEVELOPED EXAMPLE CIRCUIT (BOG 0 - LPF)



FITNESS MEASUREMENT PROCESS

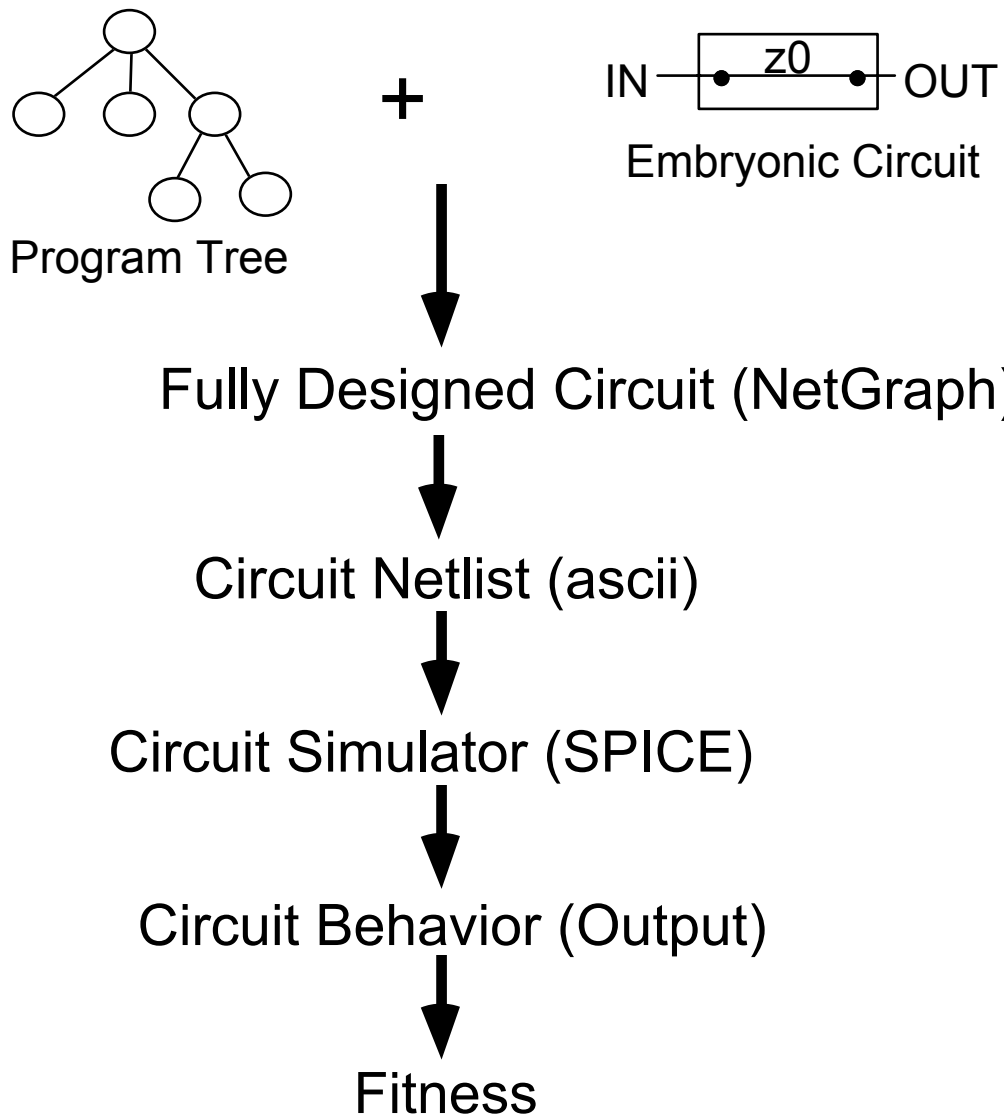

SPICE CIRCUIT SIMULATOR

- **Developed at Univ. of California - Berkeley**
- **217,000 lines of C code**
- **Hundreds of thousands of users**
- **Available in many forms from various sources (e.g., PSPICE, HSPICE)**
- **Input required by SPICE**
 - Netlist
 - SPICE Commands
 - Models
- **Types of analysis produced by SPICE**
 - Fourier
 - AC Sweep
 - DC Sweep
 - Transient
 - Operating point
 - Sensitivity
 - Distortion
 - Noise
 - Pole-Zero
 - Transfer function

SPICE NETLIST

```
Circuit Must Have a Title
V0          2  0      DC  0V
QD2         3  3  4  Q2P3906
R6          1  0      1.00e+00K
R7          2  1      1.00e+00K
QNC9        5  1  1  Q2P3906
QGE12       1  6  0  Q2N3904
QD13        1  1  4  Q2P3906
QNC15       5  3  7  Q2P3906
Q17         7  6  0  Q2N3904
VNEGQ999    5  0      DC -15V
.MODEL      Q2P3906PNP      Bf=180.7
Br=4.977
.MODEL      Q2N3904NPN      Bf=416.4
Br=0.7371
.DC V0 -0.25 0.251 0.025
.PLOT DC V(1)
.OPTIONS NOPAGE NOMOD
.END
```